

# IDP EE3025

## CALCULATOR

HRITIK N CHAVAN-EE16BTECH11012  
SWAPNIL P JOSHI-EE16BTECH11016

INDIAN INSTITUTE OF TECHNOLOGY HYDERABAD

29 MARCH 2019

# Problem Statement

- Implementation of Calculator with basic operations
  - ADDER
  - SUBTRACTOR
  - MULTIPLIER
  - DIVIDER
  - MODULUS

# Introduction

- Implementing a simple calculator which performs basic operations of addition, subtraction, multiplication , division and modulus on the given 4-bit binary number.

# Progress

We have implemented addition and subtraction by realising a full adder.

- Adder implemented by sequential addition of bits.
- Subtractor by using 2's complement of the number.

## Listing 1: ADDER-SUBTRACTOR

```
module ripple_carry_adder_subtractor(S, C, V, A, B,  
    output [3:0] S;  
    output      C;  
    output      V;  
    input  [3:0] A;  
    input  [3:0] B;  
    input      Op;  
  
    wire      C0;  
    wire      C1;  
    wire      C2;  
    wire      C3;  
    wire      B0;  
    wire      B1;  
    wire      B2;  
    wire      B3;
```

```
xor(B0, B[0], Op);  
xor(B1, B[1], Op);  
xor(B2, B[2], Op);  
xor(B3, B[3], Op);  
xor(C, C3, Op);  
xor(V, C3, C2);  
full_adder fa0(S[0], C0, A[0], B0, Op);  
full_adder fa1(S[1], C1, A[1], B1, C0);  
full_adder fa2(S[2], C2, A[2], B2, C1);  
full_adder fa3(S[3], C3, A[3], B3, C2);
```

**endmodule**

```
module full_adder(S, Cout, A, B, Cin);  
  output S;  
  output Cout;  
  input A;  
  input B;  
  input Cin;
```

```
wire    w1;  
wire    w2;  
wire    w3;  
wire    w4;  
xor(w1, A, B);  
xor(S, Cin, w1);  
and(w2, A, B);  
and(w3, A, Cin);  
and(w4, B, Cin);  
or(Cout, w2, w3, w4);  
endmodule
```

Timing diagram for the 74VHC04 inverter. The diagram shows the relationship between input A, input B, output C, output Qp, and output V over time. The input signals A and B are square waves. The output C is the inverted input A. The output Qp is the inverted input B. The output V is the inverted input A. The diagram shows that the output C is the inverted input A, and the output Qp is the inverted input B. The output V is the inverted input A.

- A AND B ARE THE INPUTS
- S IS THE OUTPUT(FINAL RESULT)
- C IS THE CARRY



# Progress

We have implemented multiplication algorithm using Vedic Multiplier.

## Listing 2: MULTIPLIER

```
module Full_Adder(input x,y,cin ,output s, cout );  
wire c1,c2,c3;  
xor(s,x,y,cin );  
and(c1,x,y),  
    (c2,x,cin ),  
    (c3,y,cin );  
or(cout,c1,c2,c3 );  
endmodule  
  
// Multiplier  
  
module M4bit(input [3:0] Q,input [3:0] M,output [7:  
wire c1,c2,c3,c4,c5,c6,c7,c8,c9,c10,c11;  
wire d1,d2,d3,d4,d5,d6,d7;  
wire e1,e2,e3;  
wire f1,f2,f3,f4,f5,f6,f7;  
wire g1,g2,g3,g4;
```

```
and(c1,M[3],Q[1]),  
(c2,M[2],Q[2]),  
(c3,M[1],Q[3]),  
(c4,M[3],Q[0]),  
(c5,M[2],Q[1]),  
(c6,M[1],Q[2]),  
(c7,M[2],Q[0]),  
(c8,M[1],Q[1]),  
(c9,M[0],Q[2]),  
(c10,M[1],Q[0]),  
(c11,M[0],Q[1]),  
(P[0],M[0],Q[0]);
```

```
Full_Adder fa1(c1,c2,c3,d2,d1);  
Full_Adder fa2(c4,c5,c6,d4,d3);  
Full_Adder fa3(c7,c8,c9,d6,d5);  
Full_Adder fa4(c10,c11,0,P[1],d7);
```

```
and(e1,M[2],Q[3]),  
(e2,M[3],Q[2]),  
(e3,M[0],Q[3]);
```

```
Full_Adder fa5(e1,e2,d1,f2,f1);  
Full_Adder fa6(d2,d3,f5,f4,f3);  
Full_Adder fa7(d4,e3,d5,f6,f5);  
Full_Adder fa8(d6,d7,0,P[2],f7);
```

```
and(g1,M[3],Q[3]);
```

```
Full_Adder fa9(g1,f1,g2,P[6],P[7]);  
Full_Adder fa10(f2,f3,g3,P[5],g2);  
Full_Adder fa11(f4,0,g4,P[4],g3);  
Full_Adder fa12(f6,f7,0,P[3],g4);
```

```
endmodule
```

	$p_{15}$	$p_{14}$	$p_{13}$	$p_{12}$	$p_{11}$	$p_{10}$	$p_9$	$p_8$	$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$
M[15:0]	1010		011		000		011		010							
P[7:0]	101000		010010		000		011100		0100100							
Q[3:0]	100		0110		0		000		010							

- M IS THE MULTIPLICAND
- Q IS THE MULTIPLIER
- P IS THE PRODUCT

# Approach

- The input numbers are given to the arduino using a keypad.
- The arduino then communicates with the raspberry pi and sends the information to be processed.
- The ico board is connected to the raspberry pi and it acts as the processing element to compute the solution.
- The solution is then transmitted to the arduino board with the help of Raspberry pi.
- Finally, the solution is displayed on the LCD screen with the help of arduino.